University of Asia Pacific

Department of Computer Science and Engineering

CSE 450: VLSI Lab

LAB REPORT

Experiment Number: 03

Experiment Title: Design and Simulation of an 8-Bit Full Adder Using NAND-Based Structural VHDL in Xilinx ISE

Submitted by:

Name: MD Rawnak Shalahen Fahim

Student ID: 22201063

Section: C1

Submitted to:

Md. Rasheduzzaman
Lecturer
Department of Computer Science and Engineering

Date of Submission: 10/25/2026

1. Title of the Experiment

Design and Simulation of a Full Adder Using NAND-Based Structural VHDL in Xilinx ISE

2. Objectives

The main objectives of this experiment are:

1. To understand the design and operation of basic digital logic gates.
2. To implement a **NAND gate using VHDL**.
3. To construct other logic gates using NAND gate instances.
4. To implement an **XOR gate using NAND gates**.
5. To design a **Half Adder using XOR and AND gates**.
6. To design a **Full Adder using two Half Adders and an OR gate**.
7. To understand **structural modeling** in VHDL.
8. To simulate the designed circuits using **Xilinx ISE**.
9. To verify the simulated outputs with the corresponding truth tables.
10. To understand hierarchical digital circuit design, where complex circuits are constructed from simpler reusable components.
11. To design and simulate an 8-bit Full Adder by cascading eight 1-bit Full Adders using structural VHDL.

3. Software and Tools Used

The following tools were used for this experiment:

- **Xilinx ISE 14.7**
- **VHDL**
- **ISim Simulator**
- Computer system for design and simulation

4. Introduction

A Full Adder is a fundamental combinational digital circuit used to perform the addition of three binary inputs. It has three inputs:

- A – First binary input
- B – Second binary input
- Cin – Carry input

and two outputs:

- Sum – Result of binary addition
- Cout – Carry output

The Boolean expressions for a Full Adder are:

$$Sum = A \oplus B \oplus C\ in$$
$$Cout = AB + (A \oplus B)Cin$$

In this experiment, the Full Adder was designed using a **hierarchical structural approach**. First, a NAND gate was implemented. NAND gates were then used to construct other basic gates. A Half Adder was constructed using XOR and AND gates, and finally a Full Adder was constructed using two Half Adders and an OR gate.

Therefore, the overall design follows the hierarchy:

NAND Gate
↓
Basic Logic Gates
↓
Half Adder
↓
Full Adder

5. NAND Gate Design

The NAND gate is a universal logic gate. A two-input NAND gate produces the inverse of the AND operation.

The Boolean expression is:

$$Y = \overline{A \cdot B}$$

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

The NAND gate was implemented using VHDL Dataflow modeling.

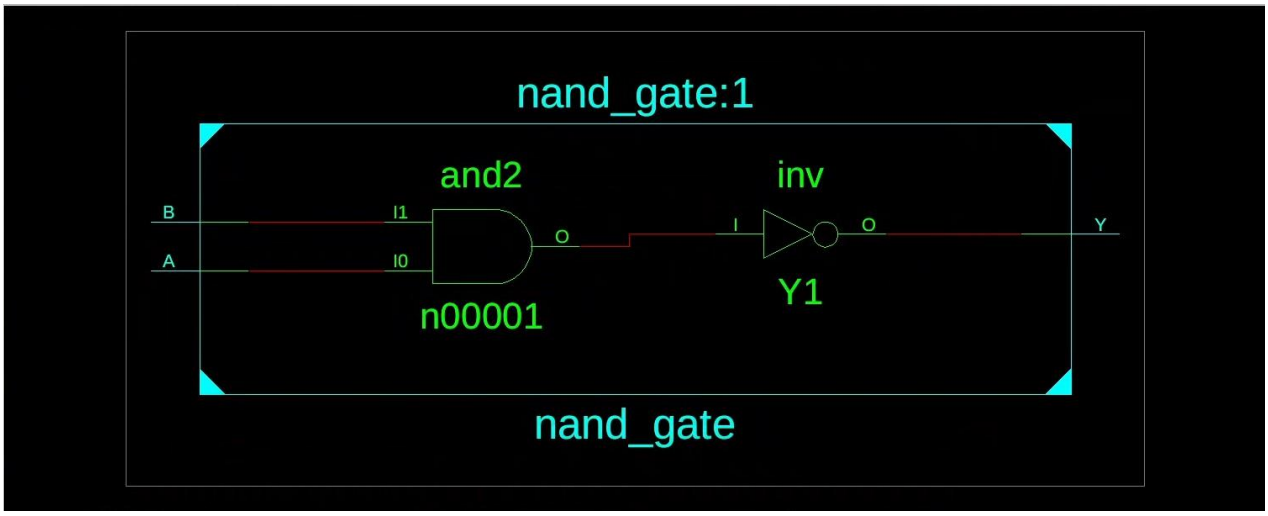


Figure 1: RTL schematic of the NAND gate.

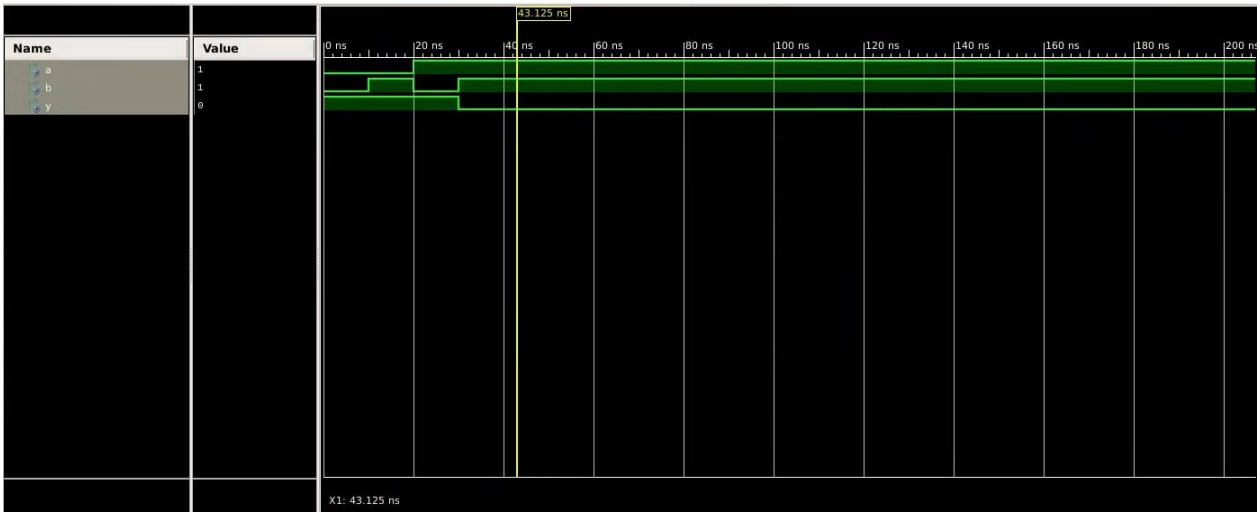


Figure 2: Simulation waveform of the NAND gate.

6. Construction of Basic Gates Using NAND Gates

Since NAND is a universal gate, other logic gates can be constructed using NAND gates.

The following gates were designed using NAND gate instances:

- AND
- OR
- NOR
- XOR

These gates were implemented using **structural VHDL modeling**.

6.1 AND Gate Using NAND Gates

An AND gate can be constructed using two NAND gates.

First:

$$N1 = ANANDB$$

Then:

$$Y = N1NANDN1$$

Therefore:

$$Y = A \cdot B$$

Number of NAND gates

2 NAND gates

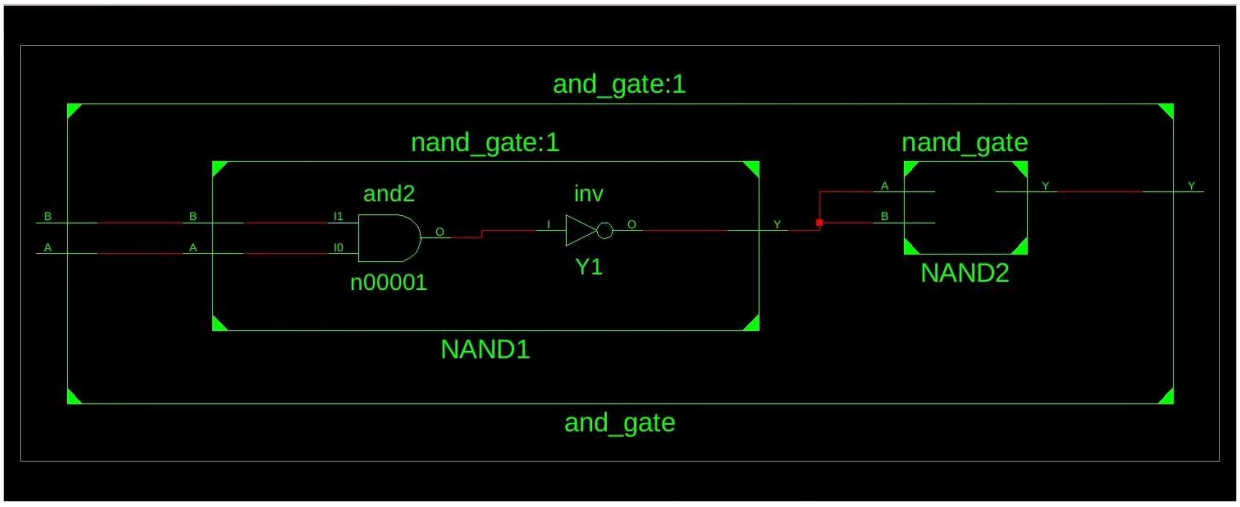


Figure 3: RTL schematic of the NAND-based AND gate.

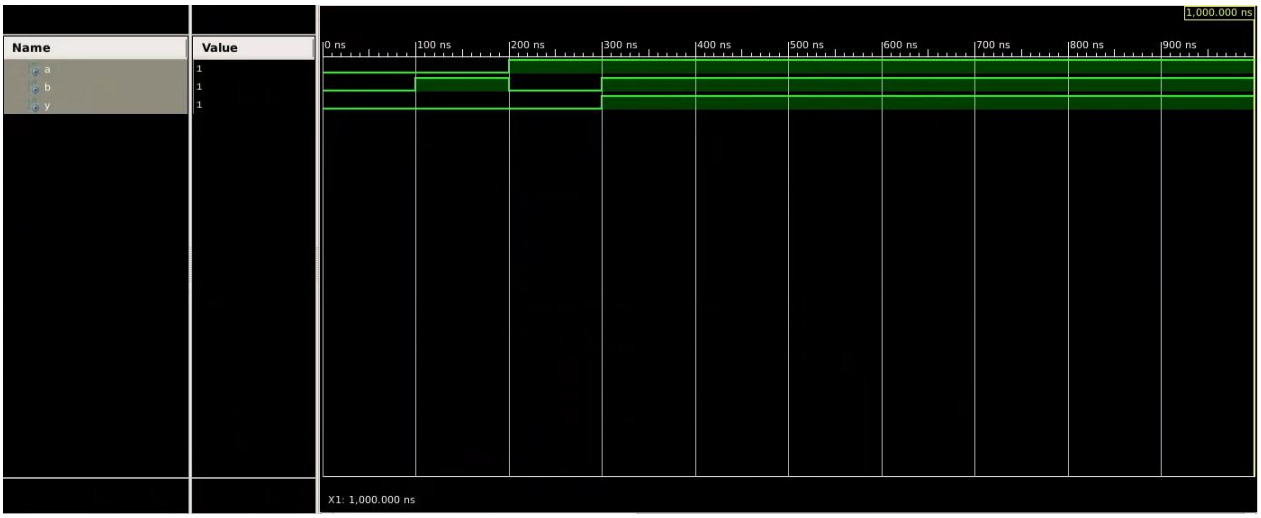


Figure 4: Simulation waveform of the AND gate.

6.2 OR Gate Using NAND Gates

Using De Morgan's theorem:

$$A + B = \bar{A}\cdot\bar{B}$$

Therefore:

N1 = A NAND A
N2 = B NAND B
Y = N1 NAND N2
Thus, an OR gate requires **3 NAND gates**.

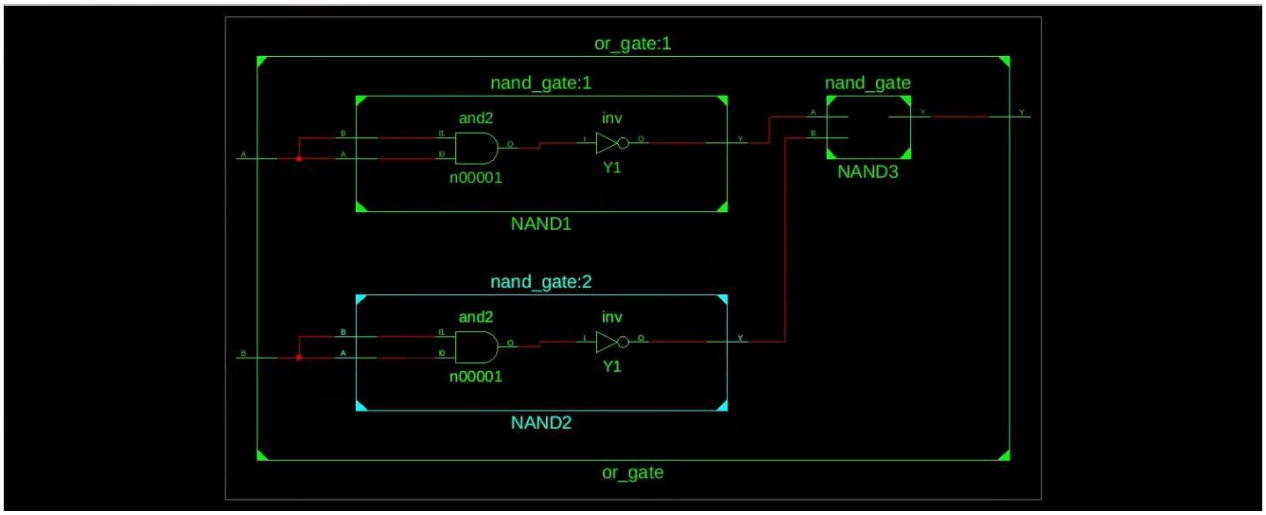


Figure 5: RTL schematic of the NAND-based OR gate.

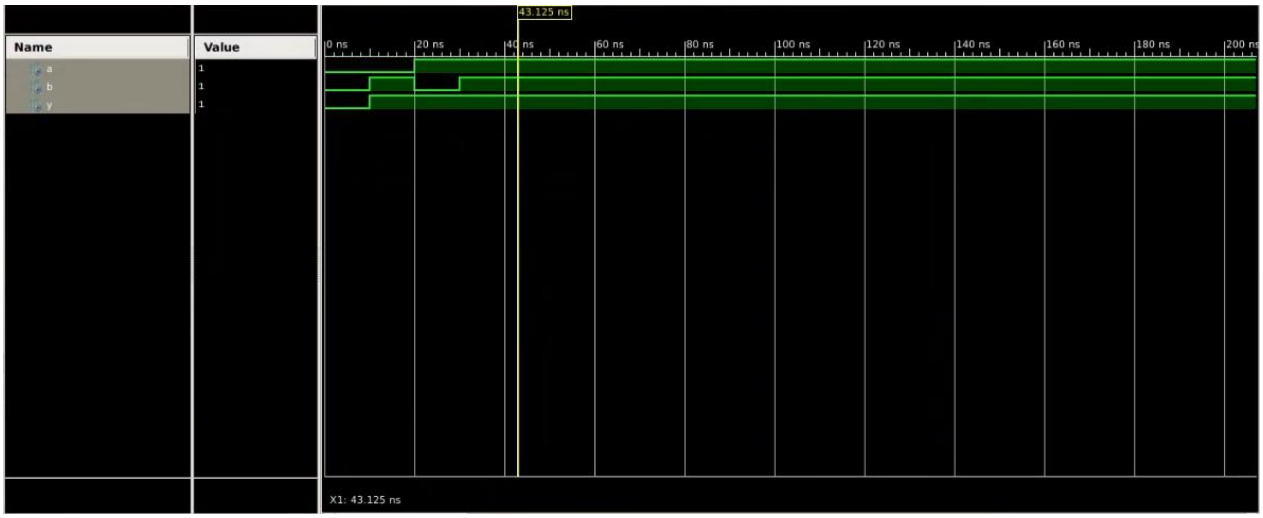


Figure 6: Simulation waveform of the OR gate.

6.3 NOR Gate Using NAND Gates

A NOR gate can be constructed by first generating an OR operation and then inverting the result.

The implementation uses four NAND gates:

N1 = A NAND A
N2 = B NAND B
N3 = N1 NAND N2
Y = N3 NAND N3
Therefore:

$$Y = A \barwedge B$$

Number of NAND gates

4 NAND gates

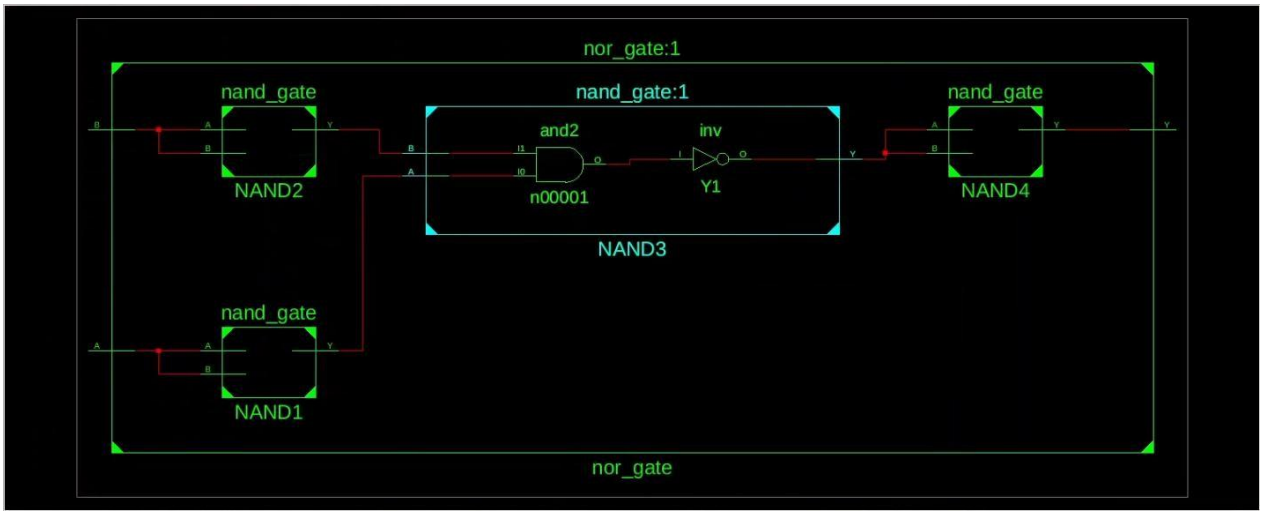


Figure 7: RTL schematic of the NAND-based NOR gate.

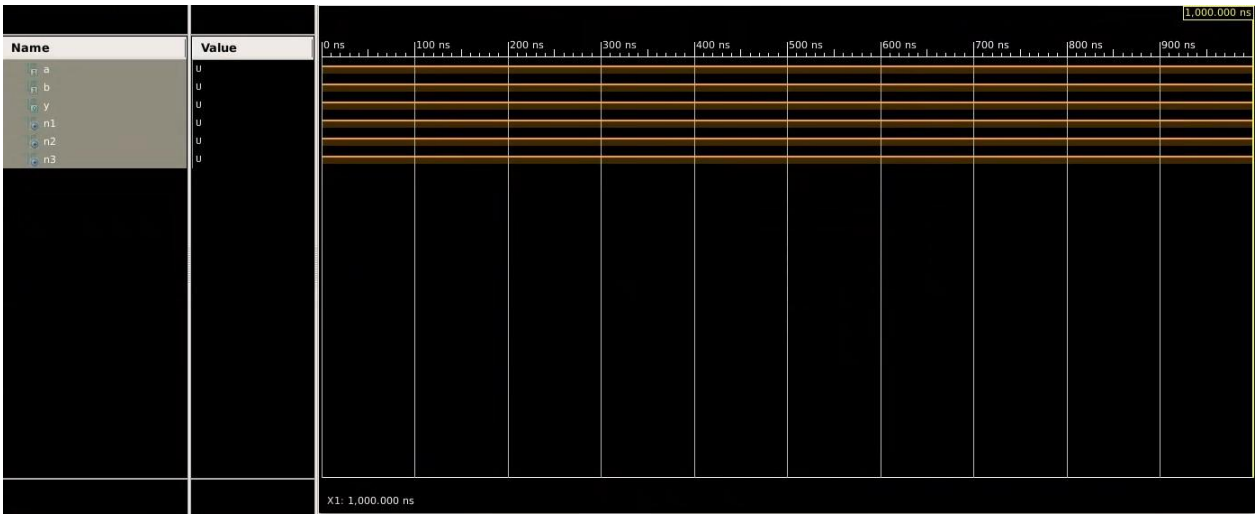


Figure 8: Simulation waveform of the NOR gate.

6.4 XOR Gate Using NAND Gates

The XOR gate produces logic 1 when the two inputs are different.

The NAND-only implementation uses four NAND gates:

N1 = A NAND B
N2 = A NAND N1
N3 = B NAND N1
Y = N2 NAND N3
Therefore:

$$Y = A \oplus B$$

Truth Table

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

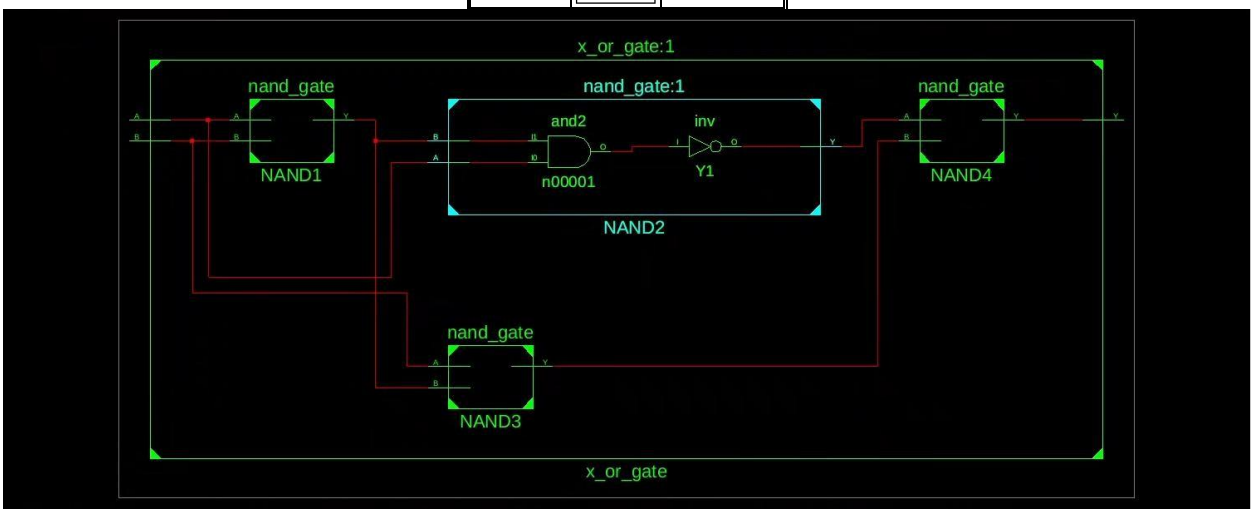


Figure 9: RTL schematic of the NAND-based XOR gate.

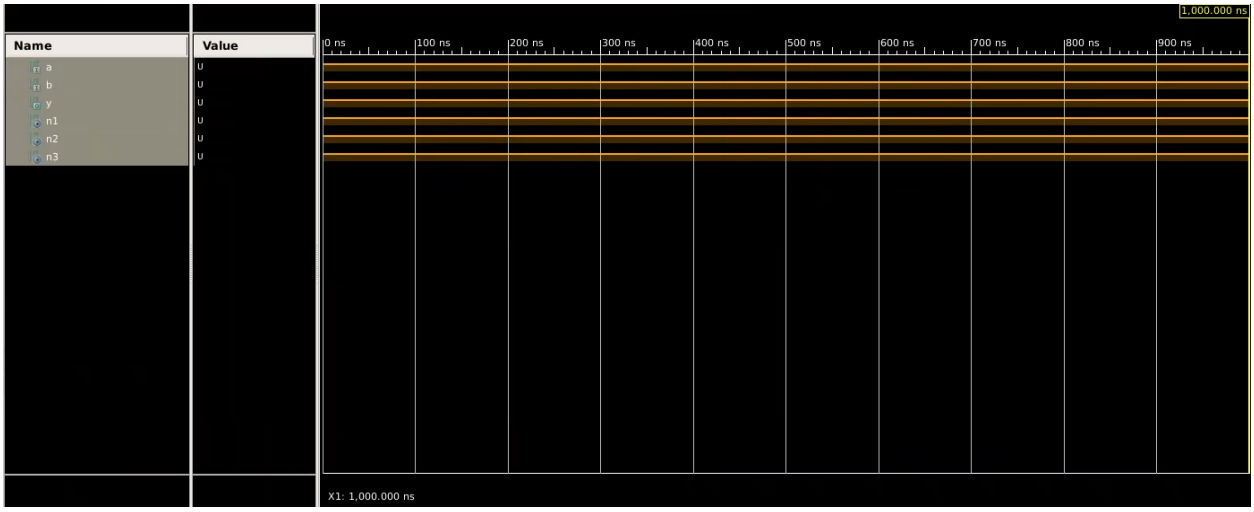


Figure 10: Simulation waveform of the XOR gate.

7. Half Adder Design

A Half Adder is a combinational circuit that adds two one-bit binary numbers.

It has:

Inputs

- A
- B

Outputs


- Sum
- Carry

The Boolean expressions are:

$$Sum = A \oplus B$$
$$Carry = A \cdot B$$

The Half Adder was implemented structurally using the previously designed XOR and AND components.

Block Diagram

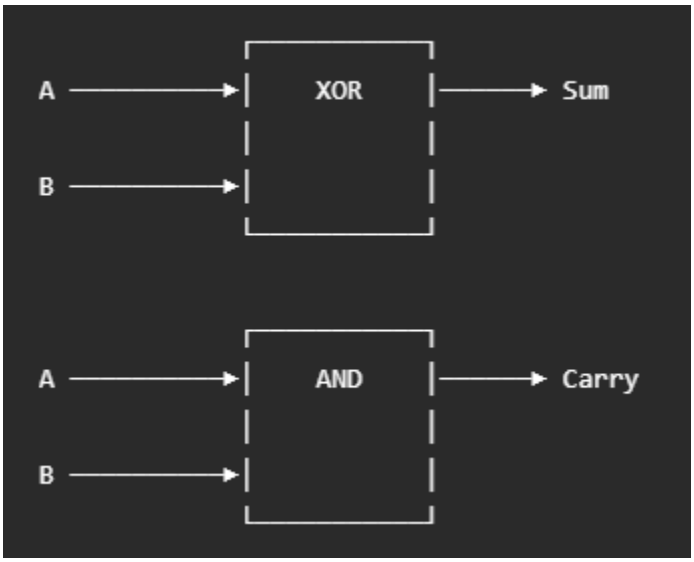

Half Adder Truth Table

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

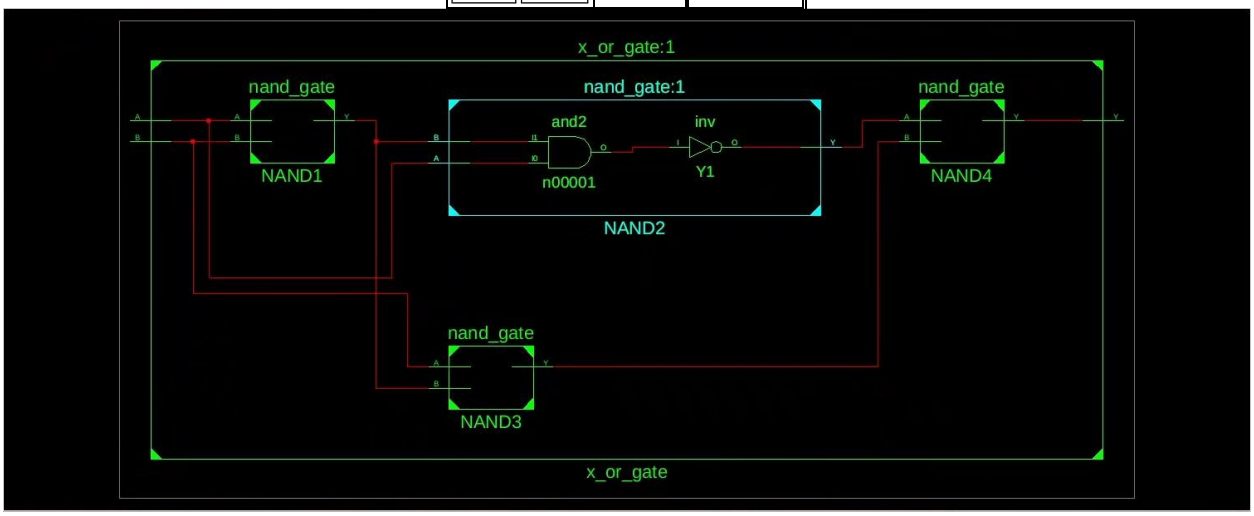


Figure 11: RTL schematic of the Half Adder.

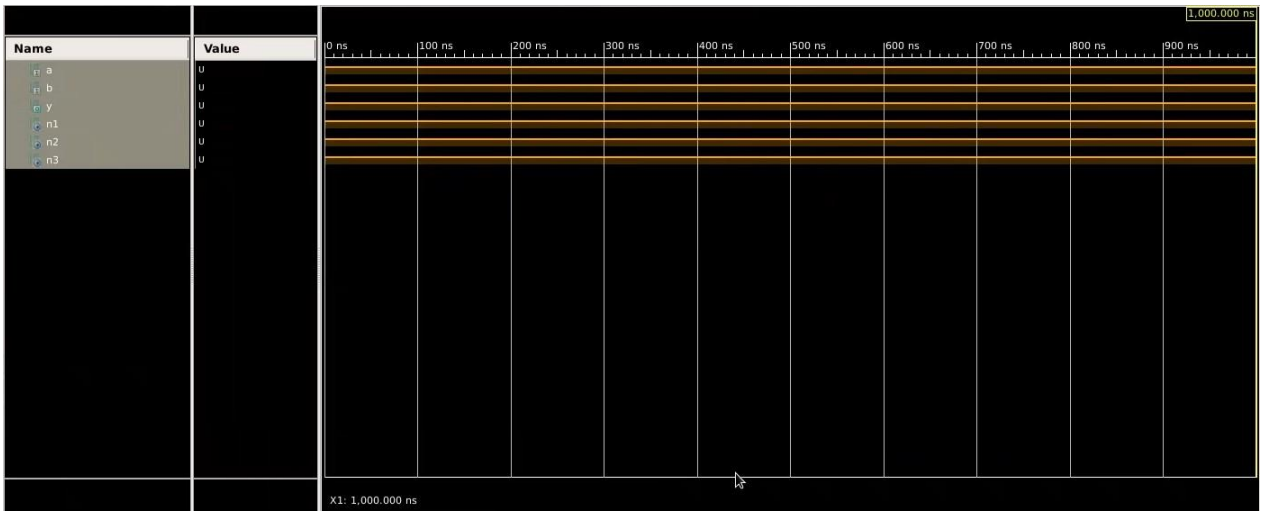


Figure 12: Simulation waveform of the Half Adder.

8. Full Adder Design

A Full Adder adds three one-bit binary values.

Inputs

- A
- B
- Cin

Outputs

- Sum
- Cout

A Full Adder can be constructed using:


- Two Half Adders
- One OR gate

The first Half Adder adds A and B.

The second Half Adder adds the intermediate sum to Cin.

Finally, the two carry outputs are passed through an OR gate.

8.1 Full Adder Block Diagram

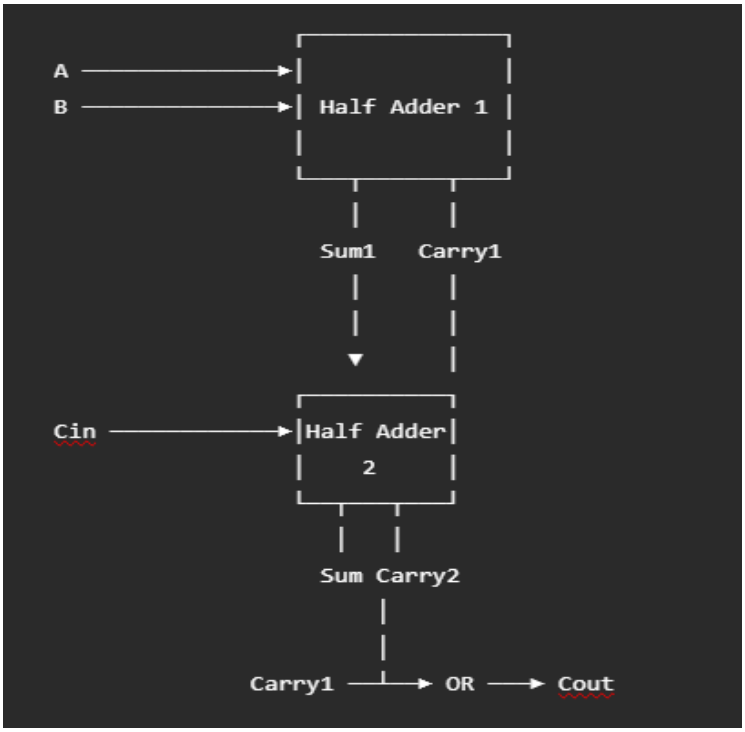

9. Full Adder Logic

The first Half Adder generates:

$$Sum1 = A \oplus B$$
$$Carry1 = A \cdot B$$

The second Half Adder generates:

$$Sum = Sum1 \oplus C\ in$$
$$Carry2 = Sum1 \cdot Cin$$

Finally:

$$Cout = Carry1 + Carry2$$

Therefore:

$$Sum = A \oplus B \oplus C\ in$$

and:

$$Cout = AB + (A \oplus B)Cin$$

10. Full Adder Truth Table

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

The simulation results should match this truth table for all eight possible input combinations.

11. RTL Schematic of the 8-Bit Full Adder

The final RTL schematic should show the hierarchical structure of the Full Adder.

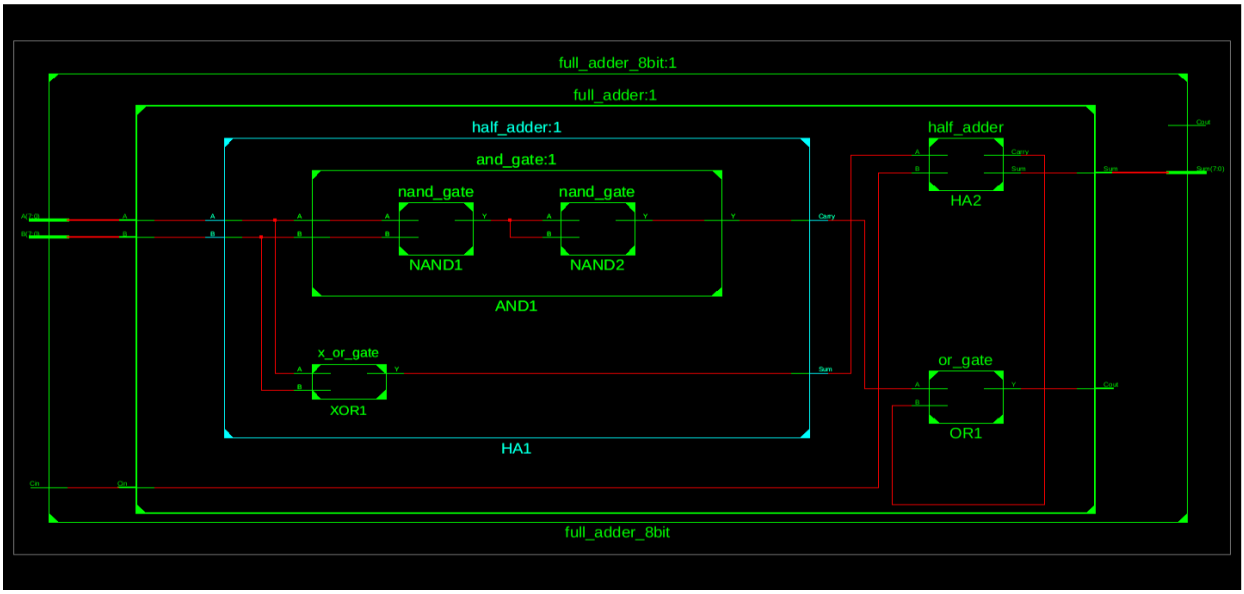


Figure 13: RTL schematic of the complete 8-bit Full Adder.

The final RTL schematic shows the hierarchical structure of the 8-bit Full Adder. Eight 1-bit Full Adders are connected in cascade, where the carry output of each stage is connected to the carry input of the next stage.

12. Simulation of the 8-Bit Full Adder

The complete 8-bit Full Adder was simulated using the ISim simulator available in Xilinx ISE. The testbench applies different combinations of two 8-bit input operands, A and B, together with the carry input Cin. The resulting 8-bit Sum and final Cout are observed from the simulation waveform.

Since the circuit is an 8-bit combinational adder, no clock signal is required. Different input combinations are applied at fixed time intervals to verify the functionality of the design.

Add this test example

A	B	Cin	Expected Sum	Cout
00000000	00000000	0	00000000	0
00000001	00000001	0	00000010	0
00000101	00000011	0	00001000	0
00001111	00001010	0	00011001	0
01100100	00110010	0	10010110	0
11111111	00000001	0	00000000	1
11111111	11111111	0	11111110	1
11111111	11111111	1	11111111	1

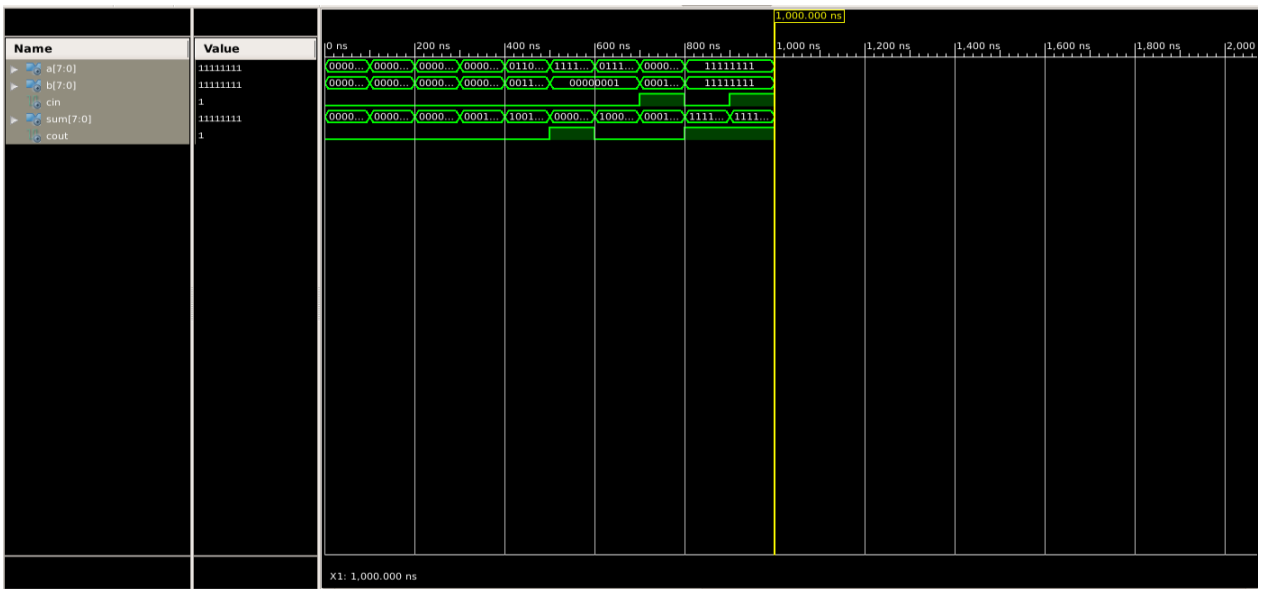


Figure 14: Simulation waveform showing all eight input combinations and corresponding Sum and Cout outputs.

For the waveform screenshot, make sure the following signals are visible:

A(7:0)

B(7:0)

Cin

Sum(7:0)

CoutIt is preferable to zoom the waveform so that all eight input combinations can be easily identified.

13. 8-Bit Full Adder Simulation Result Analysis

The simulation verifies the functionality of the designed 8 bit Full Adder.

For example:

Case 1
A = 00000001
B = 00000001
Cin = 0

Sum = 00000010
Cout = 0
Therefore:
1 + 1 = 2
Case 2
A = 11111111
B = 00000001
Cin = 0

Sum = 00000000
Cout = 1
Therefore:
255 + 1 = 256
Case 3

A = 11111111
B = 11111111
Cin = 1

Sum = 11111111
Cout = 1
Therefore:
255 + 255 + 1 = 511

The simulation results agree with the expected arithmetic results, confirming the correct operation of the 8-bit Full Adder.

14. GitHub Repository

All VHDL source codes, testbenches, and related project files should be uploaded to a GitHub repository.

GitHub Repository Link

https://github.com/Tasnim3322Abrar/ISE-14.7-for-VLSI/tree/main/8bit_full_adder

15. Conclusion

In this experiment, an 8-bit Full Adder was designed and simulated using VHDL and Xilinx ISE. The design followed a hierarchical structural approach in which a NAND gate was initially implemented and subsequently used to construct other basic logic gates.

The XOR and AND gates were then used to construct a Half Adder, while two Half Adders and an OR gate were used to construct a 1-bit Full Adder. Finally, eight 1-bit Full Adders were cascaded to construct the complete 8-bit Full Adder.

The designed circuit accepts two 8-bit binary inputs, A and B, along with an initial carry input, Cin. It produces an 8-bit Sum and a final carry output, Cout. The carry output of each Full Adder is connected to the carry input of the following stage.

The design was simulated using the ISim simulator in Xilinx ISE. Different input combinations were applied, and the resulting Sum and Cout values matched the expected arithmetic results. Therefore, the 8-bit Full Adder was successfully designed, implemented, and verified.

This experiment demonstrates the use of structural VHDL, component instantiation, hierarchical design, and reusable digital building blocks to construct a larger combinational circuit.